

# Task 3

Deep Das

Question : Differences between float and double in C++ explain with example and its

Answer :

In C++, `float` and `double` are both used to represent floating-point numbers, but they differ in their precision and range.

**Precision:** `float` is a single-precision floating-point number, which means it has 32 bits (4 bytes) to store the number, providing about 7 decimal digits of precision. On the other hand, `double` is a double-precision floating-point number, with 64 bits (8 bytes) to store the number, providing about 15-16 decimal digits of precision.

**Range:** `float` typically ranges from approximately  $1.5 \times 10^{-45}$  to  $3.4 \times 10^{38}$ , while `double` ranges from approximately  $5.0 \times 10^{-324}$  to  $1.7 \times 10^{308}$ .

Example:

```
#include <iostream>
using namespace std;

int main() {
    int n = 40;
    float factFloat = 1.0f;
    double factDouble = 1.0;

    for (int i = 1; i <= n; ++i) {
        factFloat *= i;
        factDouble *= i;
    }

    cout << "Factorial using float: " << factFloat << endl;
    cout << "Factorial using double: " << factDouble << endl;

    return 0;
}
```

Output :

Factorial using float: inf

Factorial using double: 8.15915e+047

So we can clearly see the change in the range.

Question : Explain different types of Logic gates with their truth table.

Answer :

Sure, here are the basic types of logic gates along with their truth tables:

#### **AND Gate:**

The output of an AND gate is high (1) only when all of its inputs are high (1), otherwise, it's low (0).

Truth table:

A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

#### **OR Gate:**

The output of an OR gate is high (1) when at least one of its inputs is high (1), otherwise, it's low (0).

Truth table:

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

#### **NOT Gate (Inverter):**

The output of a NOT gate is the inverse of its input. If the input is high (1), the output is low (0), and vice versa.

Truth table:

A	Y
0	1
1	0

#### **NAND Gate (NOT-AND):**

The output of a NAND gate is the opposite of an AND gate. It's low (0) only when all of its inputs are high (1), otherwise, it's high (1).

Truth table:

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

#### **NOR Gate** (NOT-OR):

The output of a NOR gate is the opposite of an OR gate. It's high (1) only when all of its inputs are low (0), otherwise, it's low (0).

Truth table:

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

#### **XOR Gate** (Exclusive OR):

The output of an XOR gate is high (1) when the number of high inputs is odd, otherwise, it's low (0).

Truth table:

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

#### **XNOR Gate** (Exclusive NOR):

The output of an XNOR gate is high (1) when the number of high inputs is even, otherwise, it's low (0).

Truth table:

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	1

